

BMC018. Analog Drum REVISION 2

Last updated February 26 2022

I Features

II Schematics

- A.Master Schematic.**
- B.Input/Decay**
- C.VCO**
- D.VCA**
- E.Power Connections.**

III Construction

- A.Parts List**
- B.The Board**

REVISION NOTES

1. LM13700 DIP package replaced with LM13700 SOIC package
2. 1K LED current limiting resistors replaced with 10K LED current limiting resistors

[Previous revision documentation here.](#)

I. Features

This module is an analog drum sound. It was designed to be built using a minimum of parts and no difficult to obtain parts. I initially was only trying to build a "disco tom" type sound, but I'm more impressed with it's bass-drum like sounds. It has the following controls:

1. Amplitude Decay
2. Frequency Modulation Decay
3. Depth of Frequency Decay
4. Baseline frequency
5. External Frequency CV Depth

It has just two inputs, one for a trigger and one for external CV. The output is normalized to the CV input to allow for self-modulation.

II. Schematics.

On the next page is the master schematic. There are highlighted sections of the master schematic that indicate what sub-circuit of the module the parts correspond to, these sub-circuits are then described on the following pages.


INPUT/DECAY

On the far left we see the wirepad marked "IN." A trigger or gate signal should be input here. The .01uf capacitor and 100K resistor to ground form a pulse shortener, making the pulse length of the input signal irrelevant. This is then input to an op-amp wired as a comparator. The output of the comparator goes to the two decay sections through a pair of 1n4148 diodes.

When the output goes high, current flows through these diodes quickly charging the 1uf capacitors. The 220 ohm resistors and 500KA pots in parallel with the capacitors provide a path for the capacitors to discharge the voltage. The higher the resistance, the more slowly the capacitors discharge.

Each capacitor is also connected to an op-amp wired as a buffer, which is outputting the capacitor's voltage onto the next stage, as well as lighting up an LED indicator. The output of the Frequency Decay section goes to the VCO, and the output of the Amplitude Decay section goes to the VCA.


VCO

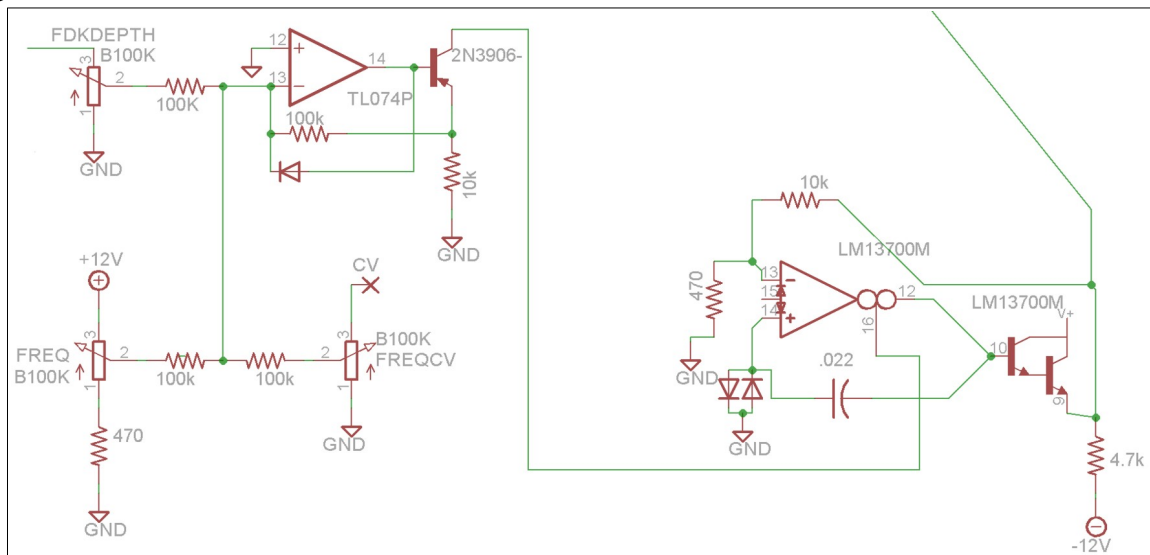


On the far left we see the input from the decay circuit. This voltage is summed with the voltages from the external frequency control and the baseline frequency control. These voltages are summed together on the negative input of the op amp wired in conjunction with a 2N3906 to form a linear voltage controlled current source.

This current source is controlling the current of one half of an LM13700 OTA wired as a VCO. The design for the VCO is taken from the LM13700 datasheet. The OTA is forming an Integrator/Schmitt Trigger type oscillator by itself.

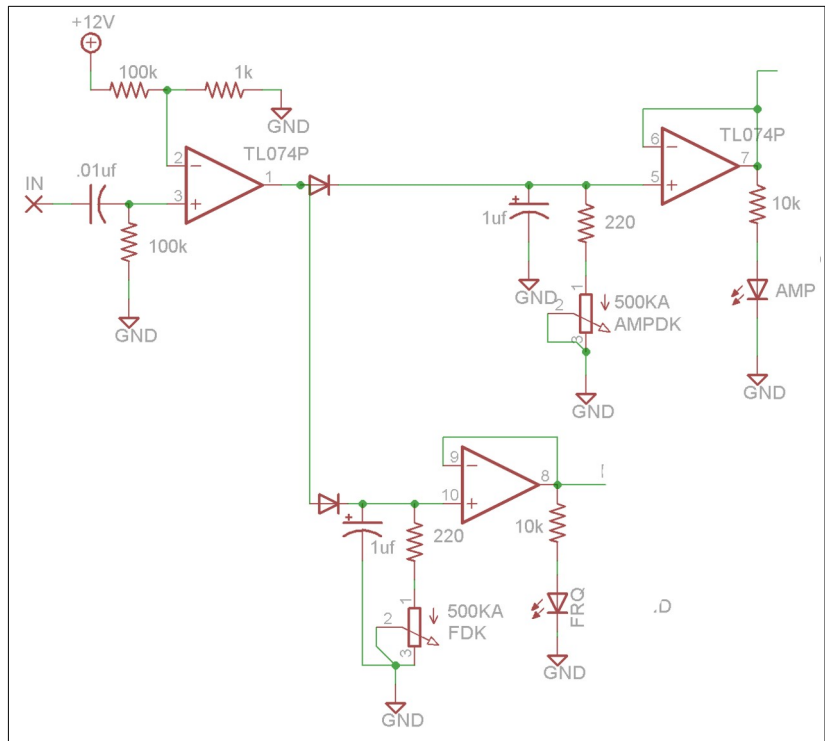IF BUILDING FOR +/-15V replace the 10K resistor in the feedback path of the OTA with a 15K. This is untested, if it works for you, or you like it more with a different value, let me know!



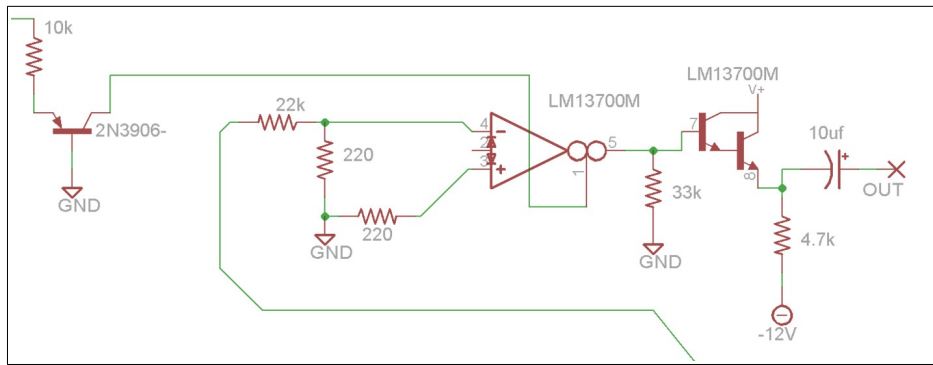


VCA

On the far left we see the output of the decay section for amplitude. A single 2n3906 in series with a 10k resistor forms the current control. This VCA is incredibly simple, the signal is input to the inverting input through a 22K and 220 ohm resistor voltage divider used to limit the signal on the input. The output of the VCA goes through the onboard buffer and then a 10uf capacitor to decouple the DC bias.

Power Connections.

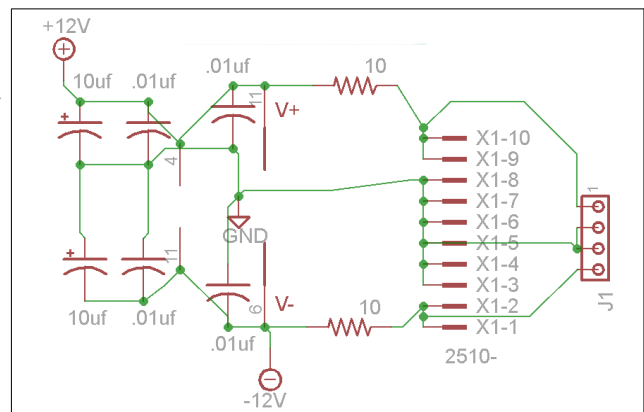Here we see the two power connectors for MOTM and Eurorack style systems. The supply is filtered by a 10 ohm resistor and 10uf capacitor, and then .01uf decoupling capacitors are placed near the power supply pins of the two ICs.



Parts List

Semiconductors

Value	Qty	Notes
TL074	1	DIP Package
LM13700M	1	SOT Package
2N3906	2	
1N4148	5	
LED	2	3mm

Resistors

Value	Qty	Notes
10 ohm	2	7.5mm lead spacing
220 ohm	4	" "
470 ohm	2	" "
1K ohm	1	" "
4.7K	2	" "
10K	5	" "
22K	1	" "
33K	1	" "
100K	6	" "
500KA Potentiometer	2	16mm pot, PCB mounted
100KB Potentiometer	3	" "

Capacitors

Value	Qty	Notes
.01uf	5	cheap ceramic 2.54mm
0.022uf	1	Poly 5mm lead spacing
1uf	2	Electrolytic
10uf	3	" "

Other

Value	Qty	Notes
Power Connector	1	Either Eurorack or MOTM
14pin DIP Socket	1	
Jacks	3	Either 1/4" or 1/8"
Knobs	5	

connect the sleeves of the jacks together.

